
# LAB 01

# COS10004 – Computer System


9/10/2021

#### **OR Gate**

 


Pin 1	Pin 2	Output
1	0	1
1	1	1
0	1	1
0	0	0

#### NOT Gate

 


Pin 1	Output
0	1
1	0

#### **NAND** Gate

 


Pin 1	Pin 2	Output
0	0	1
0	1	1
1	1	0
1	0	1

## Half Adder

 

Input 1	Input 2	Sum Output	Carry Output
1	1	0	1
1	0	1	0
0	1	1	0
0	0	0	0

## Full Adder

 

Input 1	Input 2	Carry In	Sum Output	Carry Output
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1